

SCHOOL OF ELECTRICAL ENGINEERING  
Continuous Assessment Test - II, October 2016  
B.Tech. (CSE/IT/ME/CE/ET), Fall Semester 2016

Course Code : EEE1001


Duration : 90 Minutes.

Course Name : Basic Electrical and Electronics Engg. Max. Marks : 50

*Answer all the questions.*

- 1 A series combination of 3 ohm resistance and 600 $\mu$ F capacitor in each branch [10]  
forms a three phase star connected balanced load which is connected to a  
440V, 3 Phase, 50Hz ac supply. Calculate (i) Power consumed (ii) Current  
drawn. If the same load is now connected as a delta, determine (i) The power  
consumed (ii) current drawn (iii) Give your inference on the power consumed  
in both the cases

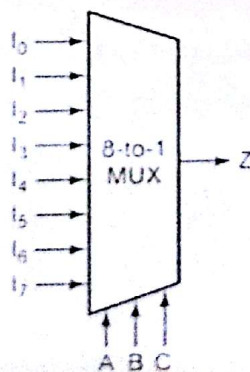- 2 Design a multiplexer for the truth table given below [10]



A	B	C	Z
0	0	0	$I_0$
0	0	1	$I_1$
0	1	0	$I_3$
0	1	1	$I_5$
1	0	0	$I_7$
1	0	1	$I_2$
1	1	0	$I_4$
1	1	1	$I_6$

- 3 Design an alarm system consisting of four Switches  $S_1, S_2, S_3, S_4$ . The alarm (A) [10]  
should sound if the switch  $S_1$  is off &  $S_2$  is on, or if  $S_1, S_2, S_3$  is on &  $S_4$  is off.  
From the truth table, obtain the minimal Boolean expression using K-Map  
and design the logic circuit with reduced expression
- 4 Design a logic circuit which receives four bit binary number and gives out an [10]  
output whenever the number is divisible by 3 or 4

- 5 a Design a circuit to add three bit numbers with two circuits adding two bit numbers [7]
- b Convert the following numbers into binary [3]
- (i)  $AE.12_{16}$  (ii)  $67.125_8$  (iii)  $10.826_{10}$