



School of Computer Science &amp; Engineering

Continuous Assessment Test – I


CSE1003-Digital Logic and Design

Time: 1:30 Hrs

Max.Marks:50

Answers ALL the questions (10×5=50 Marks)

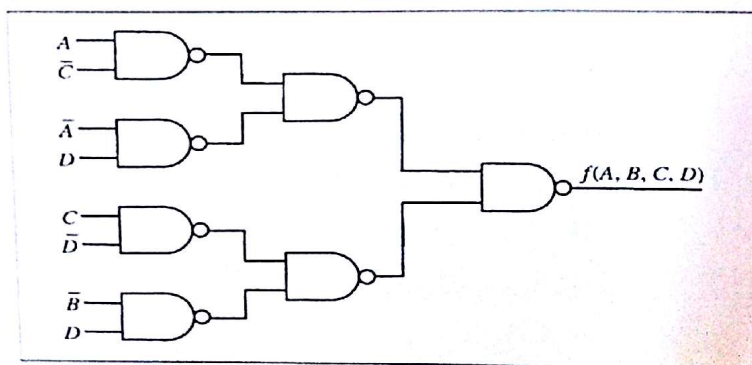1. a) The solutions to the quadratic equation  $x^2 - 13x + 32 = 0$  are  $x = 5$  and  $x = 4$ . [2]  
What is the base of the numbers?
- b) (i) Convert  $231.3_4$  to base 7. [3]  
(ii) Add -8 and +19 in 2's complement for a word length of  $n=8$ .  
(iii)  $(367)_8 * (715)_8 = \text{-----}$
2. Simplify the following Boolean functions to a minimum number of literals and draw the logic circuit for the minimized expression. [5]  
$$F(A,B,C,D) = [(A+C'+D)(B'+C)(A+B'+D)(B'+C)(B'+C+D')]'$$
3. A long hallway has three doors, one at each end and one in the middle. A switch is located at each door to operate the incandescent lights along the hallway. Label the switches A, B, and C. Design a logic network to control the lights. [5]
4. Realize the equivalent circuit using NOR gates one for the one shown below: [5]



5. Expand  $F(P,Q,R) = P + PQ + QR'$  to minterms and maxterms. [5]
6. Determine the minimum-cost POS expressions for the function [5]

$$f(A,B,C,D) = \sum m(4,6,8,10,11,12,15) + d(3,5,7,9)$$

(P.T.O)

7. Simplify the Boolean function  $F$  using the don't care conditions  $d$  in SOP [5]

$$F = w'(x'y + x'y' + xyz) + x'z'(y+w)$$

$$d = w'x(y'z + yz') + wyz$$

8. Explain the full subtractor with the neat circuit diagram. [5]
9. Reduce the expression using tabulation method and find the prime implicants [5]

$$F(A,B,C,D) = \sum(0,1,2,3,6,7,13,15)$$

10. Design a Combinational circuit that accepts a 3-bit number and generates as output a binary number equal to the square of the input number. [5]

-----ALL THE BEST-----

