

Final Assessment Test (FAT) – May 2017

Course : CSE1003 - Digital Logic and Design

Class NBR(s): 1661 / 1670 / 1679 / 1685 / 1690 / 1701 /
1715 / 1728 / 1734 / 1742 / 1743

Slot: B2

Time: Three Hours

Max. Marks: 100

Answer any TEN Questions
(10 X 10 = 100 Marks)


1. a) Formulate a weighted binary code for decimal digits using weights [5]
 - i. 6, 3, 1, 1
 - ii. 6, 4, 2, 1
- b) Represent the decimal number 5.137 in [5]
 - i) BCD
 - ii) excess-3 code
 - iii) 2421 code
 - iv) a 6311 code
2. a) The following function is in minimum sum of products form. Implement it using **only 2- input NAND** [6]
 gates. No gate may be used as a NOT gate. Show both block diagram and the equation. (You should not use more than 12 NAND gates)
 $G = A B C E' + A' B' E' + B' C' E + A' B C E + A D'$
- b) Show that the dual of the exclusive-OR is equal to its Complement. [4]
3. Minimize the following Boolean function F using Quine -McCluskey method and find the essential prime [4]
 implicants:

$$F(A, B, C, D) = \sum m(2, 3, 7, 9, 11, 13) + \sum d(1, 10, 15)$$
4. Design a circuit that counts the number of 1's present in 3 inputs A, B and C. Its output is a two-bit [4]
 number $X_1 X_0$, representing that count in binary. Assume active-HIGH logic.
5. An 8×1 multiplexer has inputs A, B and C connected to the selection inputs S_2, S_1 , and S_0 respectively. The [4]
 data inputs I_0 through I_7 are as follows:
 - a) $I_1 = I_2 = I_7 = 0; I_3 = I_5 = 1; I_0 = I_4 = D; \text{ and } I_6 = D'.$
 - b) $I_1 = I_2 = 0; I_3 = I_7 = 1; I_4 = I_5 = D; \text{ and } I_0 = I_6 = D'.$
 Determine the Boolean function that the multiplexer implement.
6. Using a decoder and external gates, design the combinational circuit defined by the following three [4]
 Boolean functions:

$$F_1 = (y' + x) z$$

$$F_2 = y' z' + x y' + y z'$$
 
$$F_3 = (x' + y) z$$
7. Design a combinational circuit that generates the 9's complement of BCD digit. [4]
8. Consider the following state diagram for a synchronous circuit with one input X and one output Z. Analyze [4]
 this state diagram and draw its circuit implementation using JK flip-flop (for state Q_0) and T flip-flop (for state Q_1).



9. a) What is the difference between serial and parallel transfer? Explain how to convert serial data to parallel and parallel data to serial. What type of register is needed? [5]

b) The contents of a four-bit register are initially 1011. The register is shifted six times to the right, with the serial input being 101 101. What are the contents of the register after each shift? [5]

10. Design a counter with T flip-flops that goes through the following binary repeated sequence: 0, 1, 3, 7, 6, 4. Show that when binary states 010 and 101 are taken to be don't-care conditions. The counter may not operate properly. Find a way to correct the design.

11. List the modes of operation of a Shift register. Illustrate the data bit flow in all the modes.

12. Write a short note on VLSI and FPGA architectures.

13. Define the carry propagate and carry generate as

$$P_i = A_i + B_i$$

$$G_i = A_i B_i$$

respectively. Show that the output carry and output sum of a full adder becomes

$$C_{i+1} = (C_i' G_i' + P_i)'$$

$$S_i = (P_i G_i') \oplus C_i$$

If the logic diagram of the first stage of a four-bit parallel adder is as shown below. Identify the P_i' and G_i' terminals and show that the circuit implements a full-adder circuit. Also Derive the Boolean functions for the lookahead carries C_2 , C_3 , and C_4 .

